

M4 Tasks:

- Lab 7 Memory Expert / Redesign memory
(Zeen) [due: 05/03/22] ✓
- Writing tests for memory
(Zeen) [due: 05/02/22] ✓
- Writing tests for 16 bit registers
(Helen) [due:05/03/2022] ✓
- Writing tests for ALU
(Jermaine) [due:05/02/22]
- Writing tests for 3-bit MUX
(Athena) [due: 05/01/22] ✓
- Writing tests for 2-bit MUX
(Jermaine) [due: 05/02/22]
- Writing tests for 1-bit MUX ✓
(Zeen) [due: 05/02/22]
- Writing tests for Shift Left
(Athena) [due: 05/01/22] ✓
- Writing tests for SE
(Athena) [due: 05/01/22] ✓
- Writing tests for ZE
(Athena) [due: 05/01/22] ✓
- Design component 2-bit MUX
(Jermaine) [due: 05/01/22]
- Design component 3-bit MUX
(Athena) [due: 05/01/22] ✓
- Design component shift left
(Athena) [due: 05/01/22] ✓
- Implementation +Testing of Integration Plan
 - PC
(Helen) [due:05/03/2022]
 - Memory
(Zeen) [due: 05/03/22]
 - ACC, SP, MDR, SHIFT, SE, ZE
(Athena) [due: 05/03/22]
 - ALU
(Jermaine) [due: 05/03/22]

Design Document

Zeen Wang, Jermaine Brown,
Helen Wang, Athena Henderson
Team: Yellow-2122a-01

Rose-Hulman Institute of Technology
CSSE 232 Computer Architecture I

[Link to the Google Doc](#)  [DesignDocument](#)

Description:

Our design uses a single register accumulator to store data and compare it to inputs. At all times we only use one register and use an allocated space in Memory for data. For our addresses we will use sign extensions to target specific places in memory to receive either data for destination. The input must have the correct first bit to target the proper place in memory.

We are going to use 2 registers, the accumulator(\$acc) and stack pointer(\$sp). The accumulator is the only register available by the programmer.

I:

Opcode	Immediate	Unused
5	8	3

AI:

Opcode	Address (rt)	Immediate
5	8	3

PC relative for bne and beq

A:

Opcode	Address (rt)	Unused
5	8	3

J:

Opcode	Address (rt)
5	11

We left shift by 1 bit then we sign extent (the most significant bit will be 1 if it is a data and 0 if it is a instruction)

Memory Map:

previous:

	0xFFFE	ra
Data	0xFF00	
Stack	0xFEFE	sp
	0x0FFE	
Text	0x0000	

new:

	0x07FE	ra
Data	0x0700	
Stack	0x06FE	sp
	0x00FE	
Text	0x0000	

Instructions:

Name	Type	Operation	Opcode
load a	A	acc = Mem[getAddr(rt)]	00001
	Takes an 8 bit address a and loads the value at memory address a to the accumulator, using the address rule. If rt = 0xFD = 11111101 (corresponding address 0xFFFC), then the memory is going to read from input		
save a	A	Mem[getAddr(rt)] = acc	00010
	Take an 8 bit address a and save the value in the accumulator into the memory with address a, using the address rule. If rt = 0xFD, then the memory is going to sent to output		
loadui imm	I	acc = {imm, 8b'0}	00011

		Takes an 8 bit immediate and load it to the upper 8 bits of the accumulator		
bne	a, imm	Al	if(acc != Mem[getAddr(rt)]) PC = PC + 2 + getAddr(imm)	00100
		Takes an 8 bit address and a 3 bit immediate. If the value stored at address a is not equal to the value of the accumulator, then jump to the address calculated from the immediate using the branch address rule.		
beq	a, imm	Al	if(acc == Mem[getAddr(rt)]) PC = PC + 2 + getAddr(imm)	00101
		Takes an 8 bit address and a 3 bit immediate. If the value stored at address a is equal to the value of the accumulator, then jump to the address calculated from the immediate using the branch address rule.		
slt	a	A	acc = acc < Mem[getAddr(rt)] ? 1:0	00110
		Compare the value in the accumulator with the value stored at address a, if the accumulator is less than a then we set the accumulator to 1, else we set the accumulator to 0.		
slti	imm	I	acc = acc < SignExtent(imm) ? 1:0	00111
		Compare the value in the accumulator with the immediate, if the accumulator is less than the immediate then we set the accumulator to 1, else we set the accumulator to 0.		
j	a	J	PC = jumpAddr(rt)	01000
		Jump to the instruction with address a, calculated using the address rule.		
jal	a	J	Mem[ra] = PC + 2 PC = jumpAddr(rt)	01001
		Jump to the instruction with address a, calculated using the address rule. Store the current PC + 2 to a fixed memory location.		
sw	imm	I	Mem[sp + SignExtent(imm)] = acc	01010
		Stored the value in the accumulator onto the stack where it is offset imm to the stack pointer.		
lw	imm	I	acc = sp + SignExtent(imm)	01011
		Stored the value from the stack where it is off offset imm to the stack pointer to the accumulator.		
ms	imm	I	sp = sp + SignExtent(imm)	01100


	Move the stack pointer with the sign extended immediate.		
sub a	A	acc = acc - Mem[getAddr(rt)]	01101
	Subtract the value stored at address a from the accumulator and store the result in the accumulator		
add a	A	acc = acc + Mem[getAddr(rt)]	01110
	Add the value stored at address a to the accumulator and store the result in the accumulator		
addi imm	I	acc = acc + SignExtent(imm)	01111
	Add the sign extended immediate to the accumulator and store the result in the accumulator		
and a	A	acc = acc & Mem[getAddr(rt)]	10000
	And the value stored at address a to the accumulator and store the result in the accumulator		
or a	A	acc = acc Mem[getAddr(rt)]	10001
	Or the value stored at address a to the accumulator and store the result in the accumulator		
ori imm	I	acc = acc ZeroExtent(imm)	10010
	Or the zero extended immediate to the accumulator and store the result in the accumulator		
loadi imm	I	acc = SignExtent(imm)	10011
	Load the sign extended immediate to the accumulator.		
getAddr = {7{address[7]}, address, 1'b0} jumpAddr = {4b'0, address, 1'b0} ZeroExtent = {8b'0, imm} SignExtent = {8{address[7]},imm} ra = 0x07FE sp start at 0x06FE			

Address rule: We left shift by 1 bit then we sign extent (the most significant bit will be 1 if it is a data and 0 if it is a instruction)


Branch address: Left shift the immediate by 1, sign extend it to 16 bits then add it to the value of the current PC plus 2.

Types:


A:

 


I:

 

AI:

 

J:

 

Call procedure:

For the callers, they are responsible to store the \$acc register value, and put the return address on the \$acc. For callees, they are responsible to restore the value in the Data memory, and callees will move the stack to store the original value of the data in the stack memory, and restore them back before return. Also, it's callee's responsibility to store the return address in the stack memory and use them for return.

Example program(s):

<u>High Level Code</u>	<u>Assembly</u>	<u>Machine Code</u>	<u>Addresses</u>
n = 6; c = relPrime(n);	loadi 6 save n jal relPrime load m save c	10011 00000110 000 00010 10000100 000 01001 00011000 000 00001 10000011 000 00010 10000111 000	0x 0066 0x 0068 0x 006A 0x 006C 0x 006E
int relPrime(int n) { int m; m = 2; while (gcd(n, m) != 1) { m = m + 1; } return m; }	relPrime: loadi 2 save m ms -6 loop: load m sw 0 save a load n sw 2	10011 00000010 000 00010 10000011 000 01100 11111010 000 00001 1000001 000 01010 00000000 000 00010 10000000 000 00001 10000100 000 01010 00000010 000	0x 0030 0x 0032 0x 0034 0x 0036 0x 0038 0x 003A 0x 003C 0x 003E

	save b load ra sw 4 jal gcd save o lw 0 save m lw 2 save n lw 4 save ra loadi 1 bne o, end load m add 1 save m j loop end: ms 6 j ra	00010 10000001 000 0x 0040 00001 11111111 000 0x 0042 01010 00000100 000 0x 0044 01001 11100111 000 0x 0046 00010 10000101 000 0x 0048 01011 00000000 000 0x 004A 00010 10000011 000 0x 004C 01011 00000010 000 0x 004E 00010 10000100 000 0x 0050 01011 00000100 000 0x 0052 00010 11111111 000 0x 0054 10011 00000001 000 0x 0056 00100 10000101 100 0x 0058 00001 10000011 000 0x 005A 01110 00000001 000 0x 005C 00010 10000011 000 0x 005E 01000 00011011 000 0x 0060 01100 00000110 000 0x 0062 01000 11111111 000 0x 0064	
<pre> int gcd(int a, int b) { if (a == 0) { return b; } while (b != 0) { if (a > b) { a = a - b; } else { b = b - a; } } return a; } </pre>	gcd: loadi 0 bne a, loop load b j ra loop: loadi 0 bne b, go j end go: load b slt a save i loadi 1 bne i, else load a sub b save a j loop else: load b sub a save b j loop end: load a j ra	10011 00000000 000 0x 0002 00100 10000000 010 0x 0004 00001 10000001 000 0x 0006 01000 11111111 000 0x 0008 0x 000A 10011 00000000 000 0x 000C 00100 10000001 001 0x 000E 01000 00010110 000 0x 0010 00001 10000001 000 0x 0012 00110 10000000 000 0x 0014 00010 10000010 000 0x 0016 10011 00000001 000 0x 0018 00100 10000010 011 0x 001A 00001 10000000 000 0x 001C 01101 10000001 000 0x 001E 00010 10000000 000 0x 0020 01000 00000101 000 0x 0022 00001 10000001 000 0x 0024 01101 10000000 000 0x 0026 00010 10000001 000 0x 0028 00010 00000101 000 0x 002A 00001 10000000 000 0x 002C 00010 11111111 000 0x 002E	

if (n == 0) { n++; } else { n = 2; }	loadi 0 bne n, else load n add 1 save n j done else: loadi 2 save n done:	10011 00000000 000 00100 10000100 100 00001 10000100 000 01110 00000001 000 00010 10000100 000 01000 00001001 000 10011 00000010 000 00010 10000100 000	0x 0002 0x 0004 0x 0006 0x 0008 0x 000A 0x 000C 0x 000E 0x 0010 0x 0012
while (n != 0) { n = n - m }	loop: loadi 0 beq n, done load n sub m save n j loop done:	10011 00000000 000 00101 10000100 100 00001 10000100 000 01101 10000011 000 00010 10000100 000 01000 00000001 000	0x 0002 0x 0004 0x 0006 0x 0008 0x 000A 0x 000C 0x 000E
int count = 0; for (int i = 0; i < n; i++) { count++; }	loadi 0 save count save i loop: beq n, done add 1 save count save i j loop done:	10011 00000000 000 00010 10000110 000 00010 10000010 000 00101 10000100 100 01110 00000001 000 00010 10000110 000 00010 10000010 000 01000 00000100 000	0x 0002 0x 0004 0x 0006 0x 0008 0x 000A 0x 000C 0x 000E 0x 0010 0x 0012
Data: 0xFF00 a(value = m) 0xFF02 b(value = n) 0xFF04 i 0xFF06 m 0xFF08 n 0xFF0A o 0xFF0C count 0xFF0E c		Stack: 0xFEFE	

RTL:

Name	Fetch	Decode		
load a	IR = Mem[PC]; PC = PC +	MDR = Mem[SE(IR[10-3]<<1)] ALUOut = PC +	Acc = MDR	

save a	2	SE(IR[10-3]<<1)	Mem[SE(IR[10-3]<<1)] = Acc	
loadui imm			Acc = IR[10-3] << 8	
bne a, imm			if(Acc != MDR) PC = ALUOut	
beq a, imm			if(Acc == MDR) PC = ALUOut	
slt a			if(Acc < MDR) Acc = 1 else Acc = 0	
slti imm			if(Acc < SE(IR[10-3])) Acc = 1 else Acc = 0	
j a			PC = ZE(IR[10-0]<<1)	
jal a			Mem[ra] = PC PC = ZE(IR[10-0]<<1)	
sw imm			ALUOut = sp + SE(IR[10-3])	Mem[ALUOut] = Acc
lw imm			ALUOut = sp + SE(IR[10-3])	Acc = Mem[ALUOut]
ms imm			Sp = Sp + (SE(IR[10-3]))	
sub a			Acc = Acc - MDR	
add a			Acc = Acc + MDR	
addi imm			Acc = Acc + (SE(IR[10-3]))	
and a			Acc = Acc & MDR	

or a			$Acc = Acc \mid MDR$	
ori imm			$Acc = Acc \mid (ZE(IR[10-3]))$	
loadi imm			$Acc = SE(IR[10-3])$	

RTL Components

1. 16-bit Registers: reg16

Input wires:

In: 16-bit bus for Input data,

E: 1-bit Enable wire,

CLK: 1-bit clock wire

Reset:

Output wire:

Out: 16-bit bus for output data

Implemented Symbols: Acc, Sp, PC, IR, ALUOut, MDR

Description: We can write to the register only when $E = 1$. It will read and write on rising edge

Test implementation: Set reset to 1 for 10 cycles then switch it back to one. Test if the output is 0. Set input to 1 while keeping the enable as 0, the output should be 1. Change enable to 1, now the output should be 1. Change the input to 2 between the rising edge and falling edge, the next falling edge should still read 1, while the next rising edge should read 2.

2. Memory: mem16

Input wires:

Addr: 16-bit bus for Memory Address,

In: 16-bit bus for Input data,

W: 1-bit Memory write control wire,

CLK: 1-bit clock wire

Output wire:

Out: 16-bit bus for output data

Implemented Symbols: Mem

Description: It will write on rising edge

Test implementation: Give a 16-bit address and set read and write to 0, should return 0. Set read to 1, the output should be the data at the given address. Set input data to a random 16 bit number then set read to 0, write to 1, on the next cycle set read to 1, the output should be the new data.

3. ALU: alu16

Input wires:

- A:** 16-bit bus for Input A,
- B:** 16-bit bus for Input B,
- OP:** 3-bit bus for ALUopcode,
- CLK:** 1-bit clock wire

Output wire:

- Out:** 16-bit bus for output data
- Zero:** 1-bit zero wire (high for 0)

Implemented Symbols: ALU

Opcode:

- 000 for And
- 001 for Or
- 010 for Add
- 011 for Sub
- 100 for Sl

Test implementation: Input 2 16-bit numbers and change the opcode every cycle, the output should be the result of and, or, add, sub, and slt. Give 0x1111 and 0x1111 and opcode 11, the zero output should be 1. Give 0xFFFF and 0x0001 that will cause an overflow and opcode 00, the overflow output should be 1.

4. 1-bit Mux: mux1b16

Input wires:

- A:** 16-bit bus for Input A,
- B:** 16-bit bus for Input B,
- OP:** 1-bit bus for opcode

Output wire:

- Out:** 16-bit bus for output data

Implemented Symbols: 1bMux

Opcode:

- 0 for A
- 1 for B

Test implementation: Give two different 16-bit numbers, change the opcode every cycle and check the output

5. 16-bit Sign Extend: se16

Input wires:

In: 8-bit bus for Input,

Output wire:

Out: 16-bit bus for output data

Implemented Symbols:

Test implementation: Give a 8-bit number that starts with 1, should fill the upper bits with 1. Give an 8-bit number that starts with 0, should fill the upper bits with 0.

6. 16-bit Zero Extend: ze16

Input wires:

In: 8-bit bus for Input,

Output wire:

Out: 16-bit bus for output data

Implemented Symbols:

Test implementation: Give different 8-bit numbers, some starting with 1 and some startin with 0. The zero-extender should fill the upper bits with 0.

7. 1-bit Mux mux1b1

Input wires:

A: 1-bit for Input A,

B: 1-bit for Input B,

OP: 1-bit for opcode

Output wire:

Out: 1-bit for output data

Implemented Symbols:

Opcode:

0 for A

1 for B

Test implementation: Give different 1-bit numbers, set op to 1, then set op to 0

Integration Plan:

1. PC:

The first one will be small, including a 2-bit mux and PC ensuring that the mux is properly selecting the correct inputs based on the PCSrc and that the PC is changing when it should. When doing beq we will set Branch to 1 and bne/beq to 1. When doing

bne we will set Branch to 1 and bne/beq to 0. This and PCWrite will select when PC will be changed.

Input Wires:

- 2-bit PCSrc wire
- 1-bit Zero? Input
- 1-bit Branch? wire
- 1 bit bne/beq wire
- Three 16-bit bus for Input data
- 1-bit PCWrite wire
- 1-bit clock wire

Output Wires:

- 16-bit bus for output data

Tests:

Give 3 separate values for the inputs and for each value of PCSrc the clock will do 2 cycles to test when PCWrite is off or on. When PCWrite is on the output should be the selected input from the mux and if PCWrite is off the output should be the previous cycle's output. Next, set PCWrite to 0, Branch to 1 and bne/beq to 1 and check the output. Then switch bne/beq = 0 and check the output.

2. Memory:

The Second will be MEM, a 1-bit mux, and a 2-bit mux. Once again checking the mux functionality. However, this subsystem will ensure that the control of memwrite and memread are working properly with Mux outputs and that the memory block of our Datapath is working.

Input Wires:

- 1-bit MemAddr wire
- 1-bit MemData wire
- Four 16-bit bus for Input data
- 1-bit Memory write control wire
- 1-bit clock wire

Output Wires:

Link to the Google Doc  *DesignDocument*

16-bit bus for output data

Tests:

We will once again create 4 unique values for the bus inputs to use for this test. MemAddr will increment every 8 cycles while MemData increments every 4 clock cycles to test MemRead and MemWrite together for all possible combinations of the selected values.

3. Wires:

The Third subsystem will take a single input and test output for the IR, MDR, SE <<1, SE, ZE <<1, ZE, <<8, the ACCSrc 3-bit mux, ACC, and SP. This subsystem ensures a functional modification of data via bit shifts and Zero and Sign extensions, and that this modified data is properly selected and stored in the ACC and SP when it should be.

Input Wires:

3-bit ACCSrc wire

1-bit ACCWrite wire

1-bit SPWrite wire

Two 16-bit bus for Input data

1-bit clock wire

Output Wires:

16-bit bus for ACC output data

16-bit bus for SP output data

16-bit bus for MDR output data

16-bit bus for IR ZE <<1 output data

16-bit bus for IR SE <<1 output data

16-bit bus for IR SE output data

16-bit bus for IR ZE output data

Tests:

The main focus of testing the subsystem is not the ZE, SE, or bit shift since they are tested individually. The tests will increment through selections for ACCSrc every 2 cycles to alternate ACCWrite and confirm the proper outputs. At the same time SPWrite will alternate for a secondary check.

4. ALUPath:

The Fourth subsystem will include the ALUSrcA, ALUSrcB, ALU, and ALU out. This subsystem guarantees the ALU operations being performed correctly, and the output is stored with no issue.

Input Wires:

2-bit ALUSrcA wire

3-bit ALUSrcB wire

Six 16-bit bus for Input data

3-bit bus for ALUopcode

1-bit clock wire

Output Wires:

Two 16-bit bus for output data

1-bit Zero? output data

Tests:

2 of the 6 inputs are going to be the same to test Zero?. But the 6 inputs will remain the same through the test. We'll increment ALUSrcA every time we try every op code with every selection in ALUSrcB to assure that the ALUOut and ALU are working with proper selection. When we select subtract in the opcode and the 2 inputs that are valued the same we will check that Zero gives a 1 as an output.

5. Overall Integration


Finally you test the four subsystems left as one whole system by connecting the Outputs to the inputs in order that the subsystems are listed like output of PC to inputs of Memory as shown in the Datapath. Lastly connect the last output to the inputs of the PC subsystem. With tests written for the subsystems the tests for the integration are extremely similar.

Input/Output/Control:

Name:	Bit Size:	I/O/C	Description:
PCSrc	2	Control	Used to determine between ALU output, the zero-extended immediate shifted by 1, and ALUOut for the input to PC.
MemAddr	2	Control	Used to determine between PC, the sign-extended immediate shifted by 1,

			0xFFFFE, and ALUOut for the address we are writing to in memory
MemData	1	Control	Used to determine between Acc output and PC for input to memory
MemRead	1	Control	Is 1 when we are reading from memory, 0 otherwise
MemWrite	1	Control	Is 1 when we are writing to memory, 0 otherwise
SPWrite	1	Control	Is 1 when we are writing to Sp, 0 otherwise
ACCSrc	3	Control	Used to determine between the immediate shifted by 8, MDR output, data from memory, the sign-extended immediate, or Sp output for the input to the accumulator
ACCWrite	1	Control	Is 1 when we are writing to the accumulator, 0 otherwise
ALUSrcA	2	Control	Used to determine between PC, Acc output, and Sp output for the input to A
ALUSrcB	3	Control	Used to determine between 2, the sign-extended immediate, MDR output, the zero-extended immediate, and the sign-extended immediate shifted by 1 for the input to for B
Zero?	1	Control	Flag that is set to 1 when the output of the ALU is zero
ALUOp	3	Control	Used to determine which operations should be done by the ALU [000 - And, 001 - Or, 010 - Add, 011 - Sub, 100 - Slr]
Bne/Beq	1	Control	Used to determine what control bit gets passed into the PC to determine exactly when to write to the PC (specifically for determining bne/beq) [1 - Beq, 0 - Bne]
PCWrite	1	Control	Used to determine what control bit gets passed into the PC to determine exactly when to write
Branch	1	Control	Used to determine what control bit gets passed into the PC to determine exactly when to write (specifically if it's a branch instruction)

Datapath:

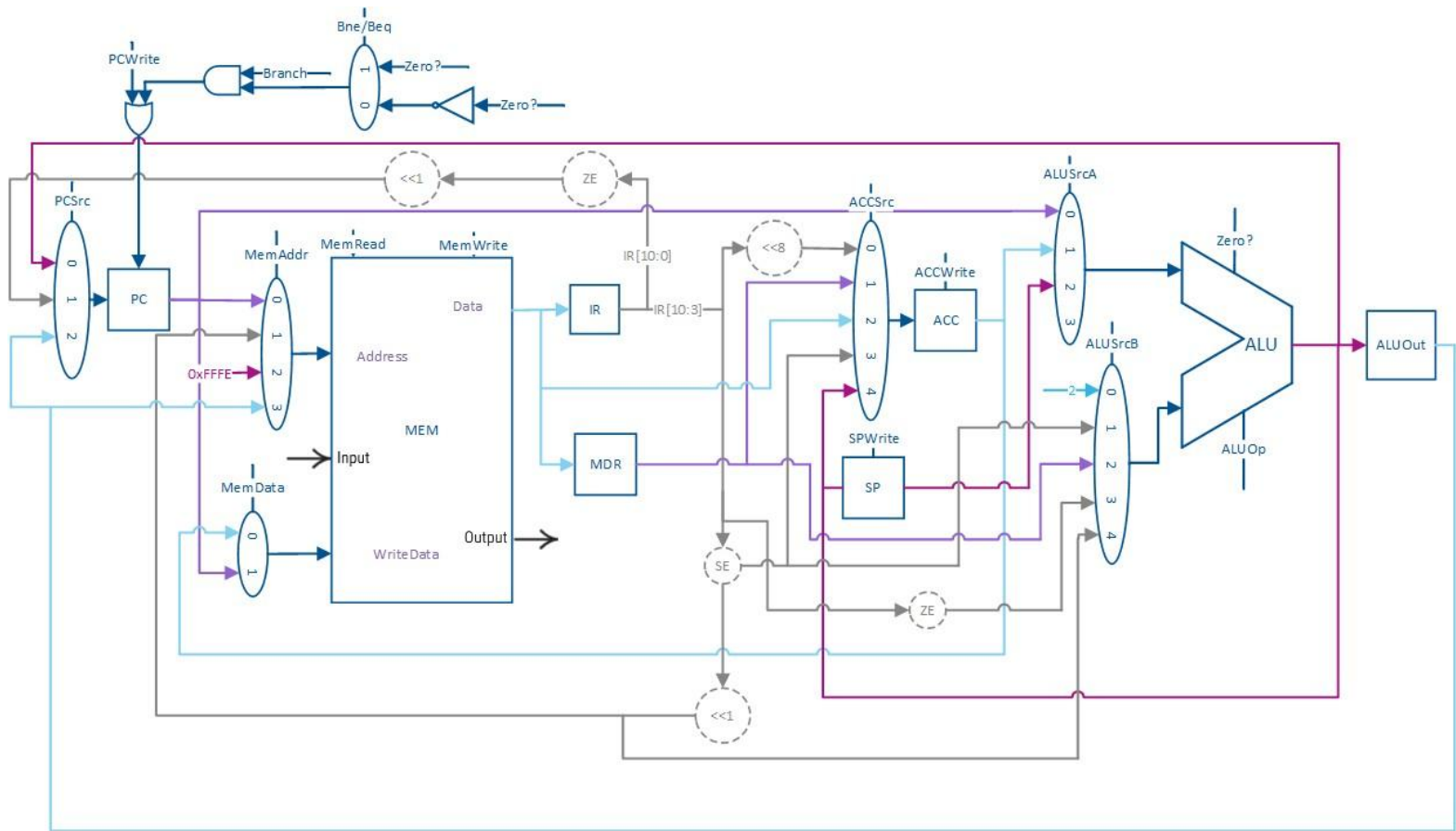


```
//Test loadui  
loadui a  
save io
```

```
//Test bne
```

```
//Test beq
```

```
//Test slt  
load a  
slt b  
save io  
load b  
slt a  
save io
```

```
//Test slti  
load a  
slt
```